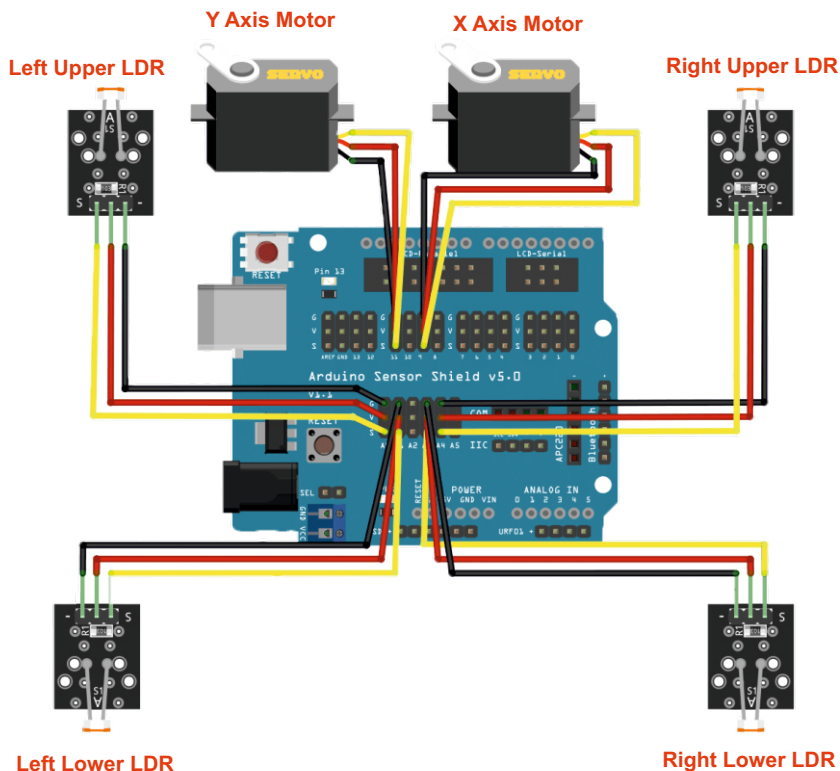


# Circuit Diagram



If there is a part that is not understood in the circuit diagram, you can see the pin numbers of all the connections in the table below. You can make your connection based on the table.

**LDR Connection Table**

A0	Top Left
A1	Bottom Left
A3	Bottom Right
A4	Top Right

**Servo Motor Connection Table**

9	X Axis Servo Motor
10	Y Axis Servo Motor